

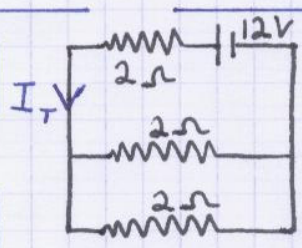
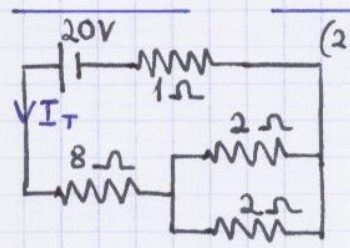
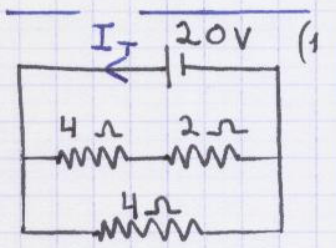
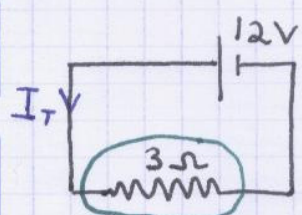
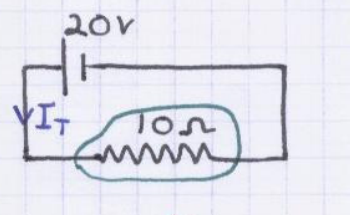
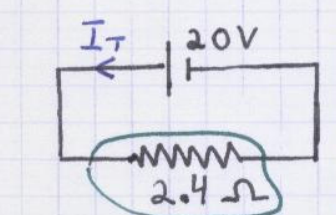
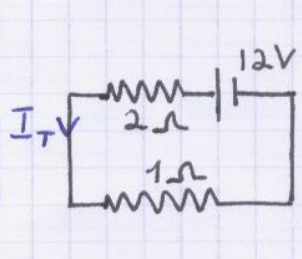


①

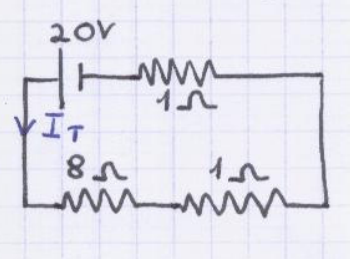


(3) ②

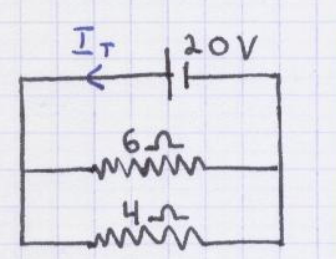


$I_T = \frac{V}{R_T} = 8\frac{1}{3} A$

$I_T = \frac{V}{R_T} = 2 A$


$I_T = \frac{V}{R_T} = 4 A$

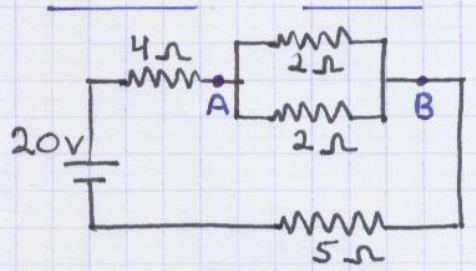

(1)


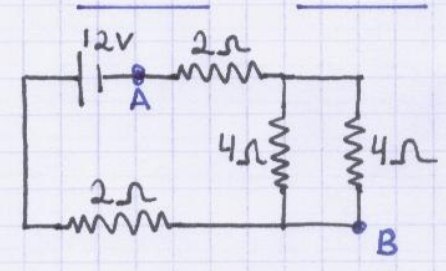


(2) ③

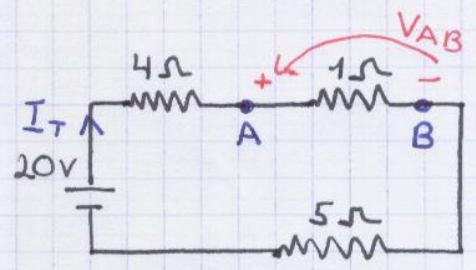

$I_T = \frac{V}{R_T} = 2 A$

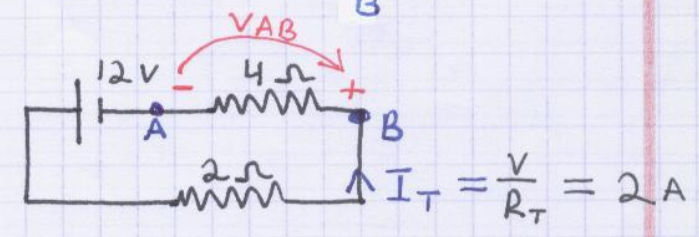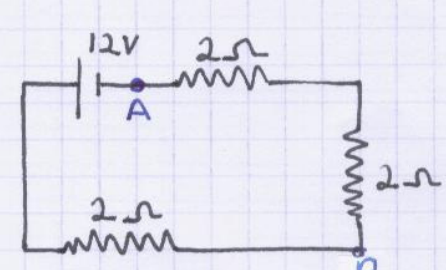$V_{AB} = I_T \cdot R_{AB} = 2 \cdot 1 = 2V$



$V_{AB} = I_T \cdot R_{AB} = 8V$