

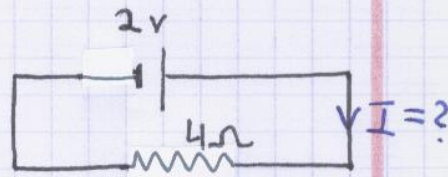
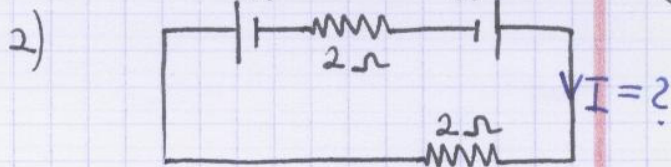


$$I = \frac{V}{R} = 1A$$

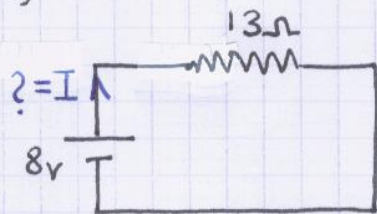



$$I = \frac{V}{R} = 0.5A$$

(4)

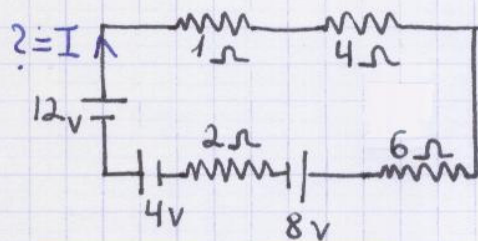

$$I = \frac{V}{R} = \frac{8}{13} A$$

(5)

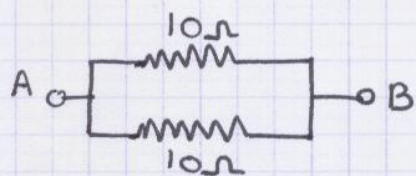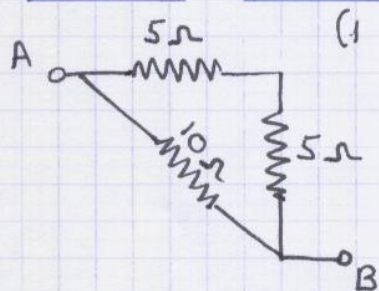

$$A \text{ --- } 5\Omega \text{ --- } B$$

